

Cryogenic Adiabatic Transistor Circuits (CATC) for Quantum Computer Control

International Symposium on Roadmapping Devices and Systems
May 27, 2021

Erik P. DeBenedictis
Zettaflops, LLC

(Based on WOLTE14 Presentation)

Summary

- Quantum computer scaleup is limited by the dissipation of classical electronics.* Digital addressed in this talk
 - CMOS means (1) transistors and (2) a circuit
 - Idea: Frank's S2LAL at cryo temperatures → Q2LAL
- Benefits:
 - ~1/1,000 heat in the cryostat
 - Lower noise in terms of power/amplitude
 - Noise can be below qubit control frequencies
 - Example cryo FPGA hybrid (e. g. reconfigurable logic)
- See <https://zettaflops.org/isrds>
 - These slides; full paper with simulation code, more

* Ref. Intel Horse Ridge lists digital and analog power about the same


Use Case: Classical Control of Quantum Computers

- Some classical functions should be near qubits
 - Set to $|0\rangle$ by measure and conditional NOT
 - Quantum error correction
 - Magic state factories

- Example


- Classical automata with 4 branches and a look-up table
- Blocks 1-2 dozen gates
- The number of automata scales, but their complexity does not

5-bit code arXiv:1705.02329:

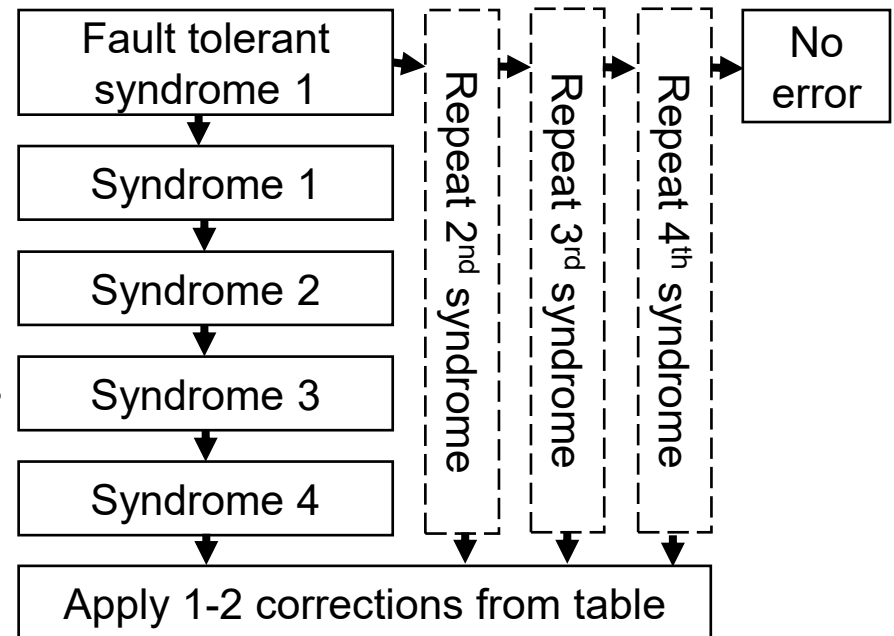

Adiabatic Circuits

 - Energy/op vs. clock period
- CMOS constant energy/op
- Adiabatic energy per op drops with clock period
- 1000× energy efficiency increase reasonable




Quiet 2 Level Adiabatic Logic

Q2LAL power-clocks


- Ramped power-clocks charge transistors gates
- No abrupt charging

①

 

 
Q2LAL power train

- Power-clocks charge transistor gates) and then leave by reflection




Even-load Adiabatic Logic Family Based on Cyber Security


(a) Circuit reference

 

(b) S2LAL signaling

 


(d) Q2LAL signaling

 


(c) S2LAL + inverter

Cumulative dissipation

 

(e) Q2LAL + inverter

Cumulative dissipation

 

Data-enabled Clocks

Effect #1: Avoid current spikes


Substantial Flat Regions

Limited
Max Slope

See Mike Frank's talk, this workshop

Effect #2: Preemphasis to reverse effect of distortion in signal transmission

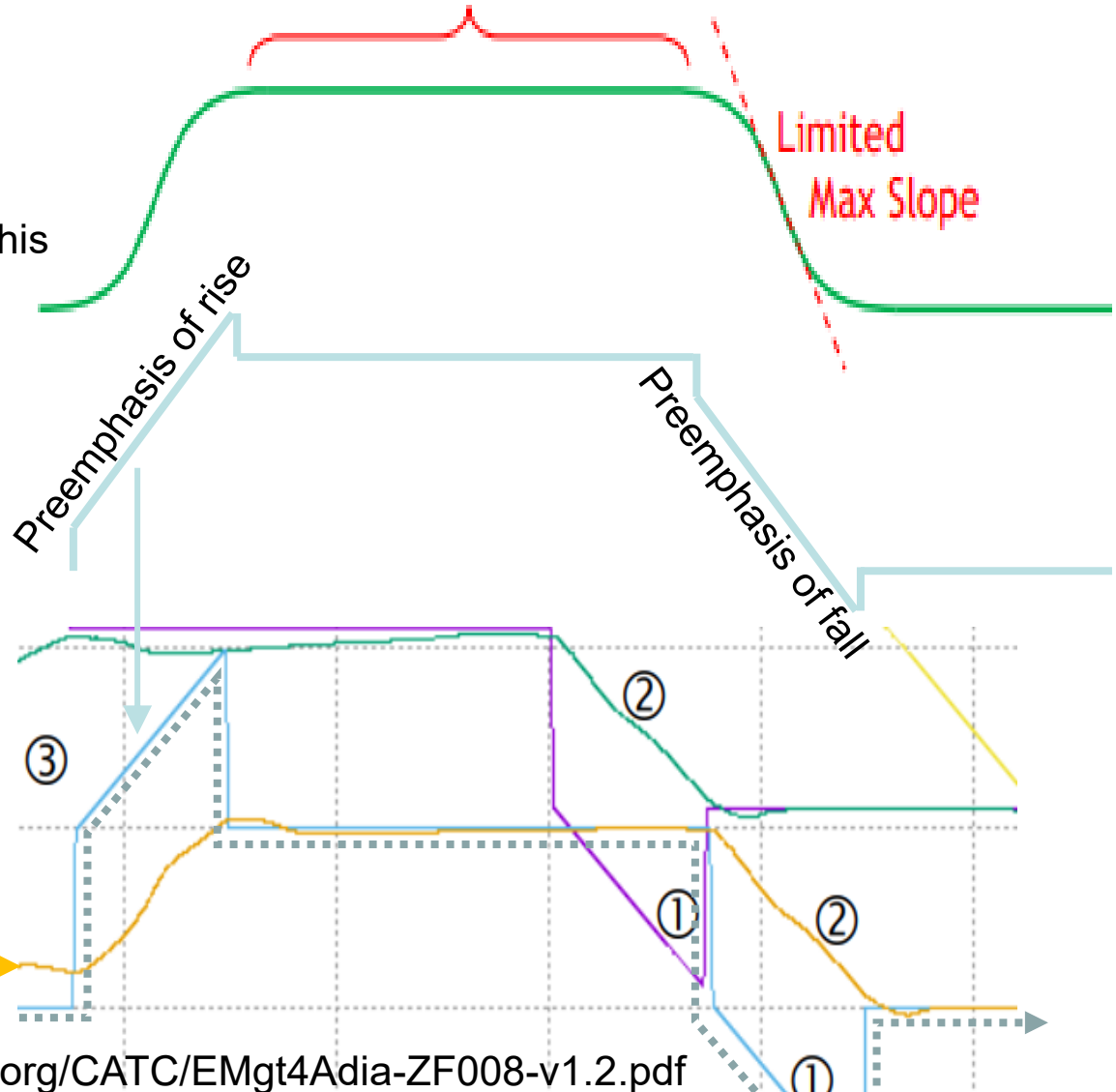Simulation: Drive 500 loads in parallel through three feet of CATV transmission line




See: <https://ar.zettaflops.org/CATC/EMgt4Adia-ZF008-v1.2.pdf>


CMOS vs. CATC noise

- CMOS noise from delta functions with frequencies determined by devices
- CATC Noise from clock
- Below same vertical but 15× expanded horizontal scale

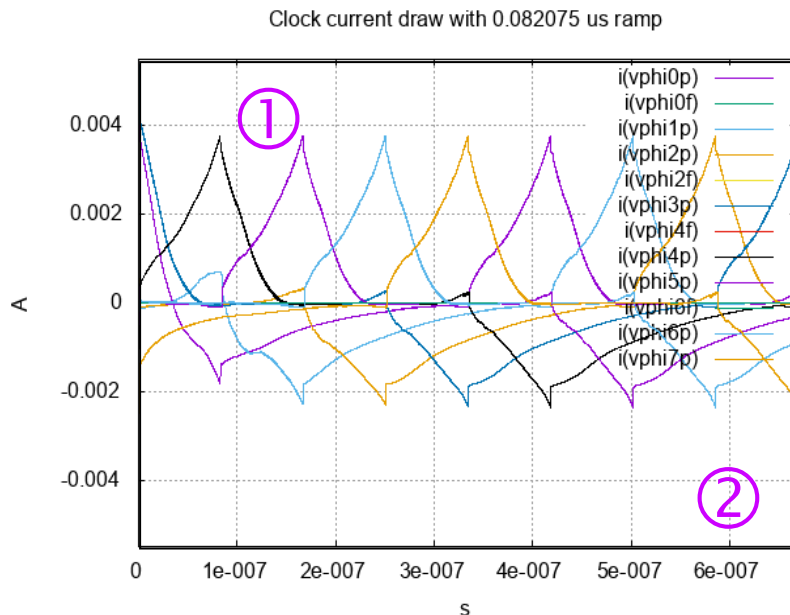(a) Power-clock current at a reference clock period




 (b) Power-clock current at 15× clock period




Data-enabled Clocks

(a) Data-enabled clock waveforms

 


- A Q2LAL circuit that can gate a Q2LAL clock on and off
- Key to implementing automata

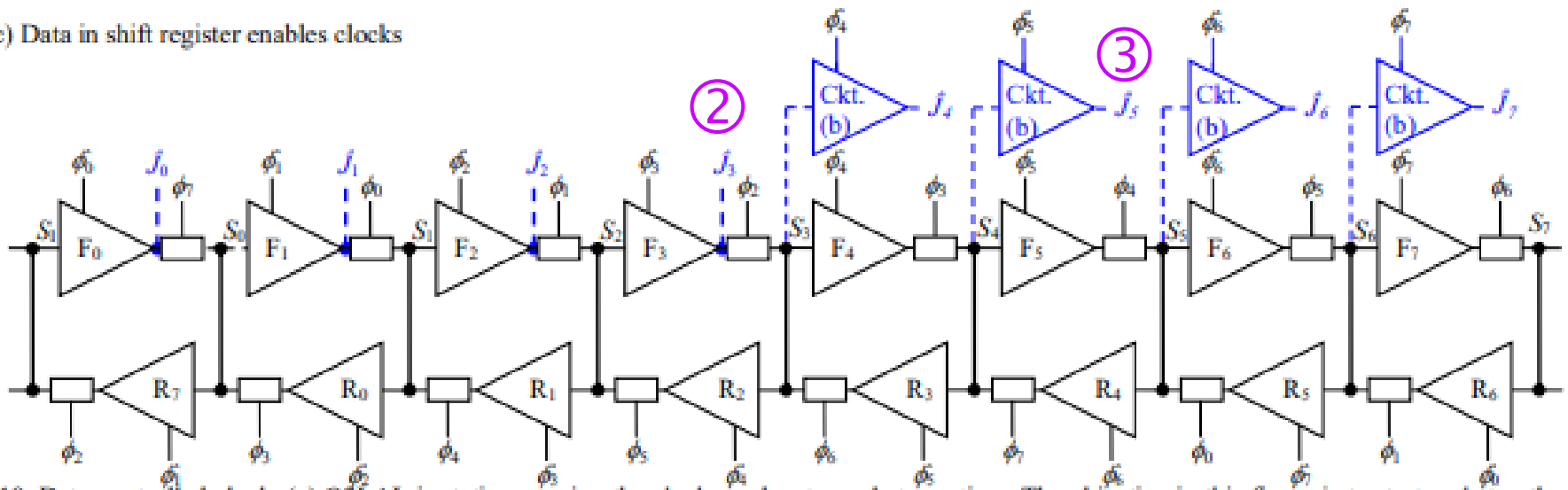(c) Data in shift register enables clocks




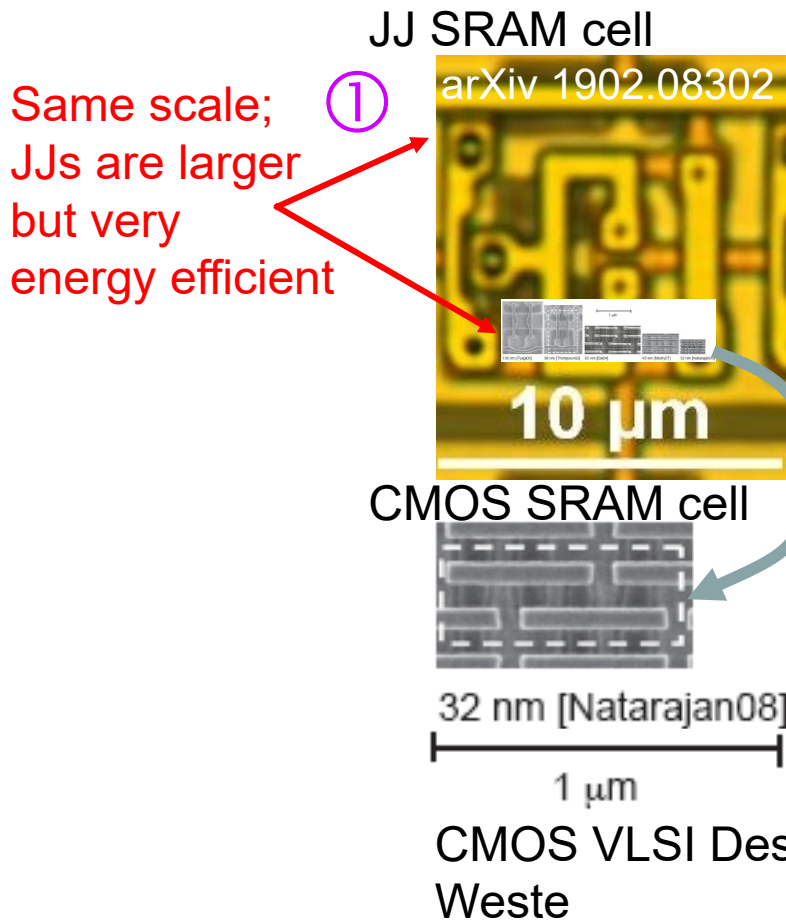Single Flux Quantum (SFQ) and CATC Hybrid



- CATC vs. JJ/SFQ
 - ② – CATC 1000 \times smaller
 - Same energy
 - CATC 1000 \times slower
- Why would you want JJs plus a lot of slow transistors?
 - ③
 - Memory
 - Complex logic

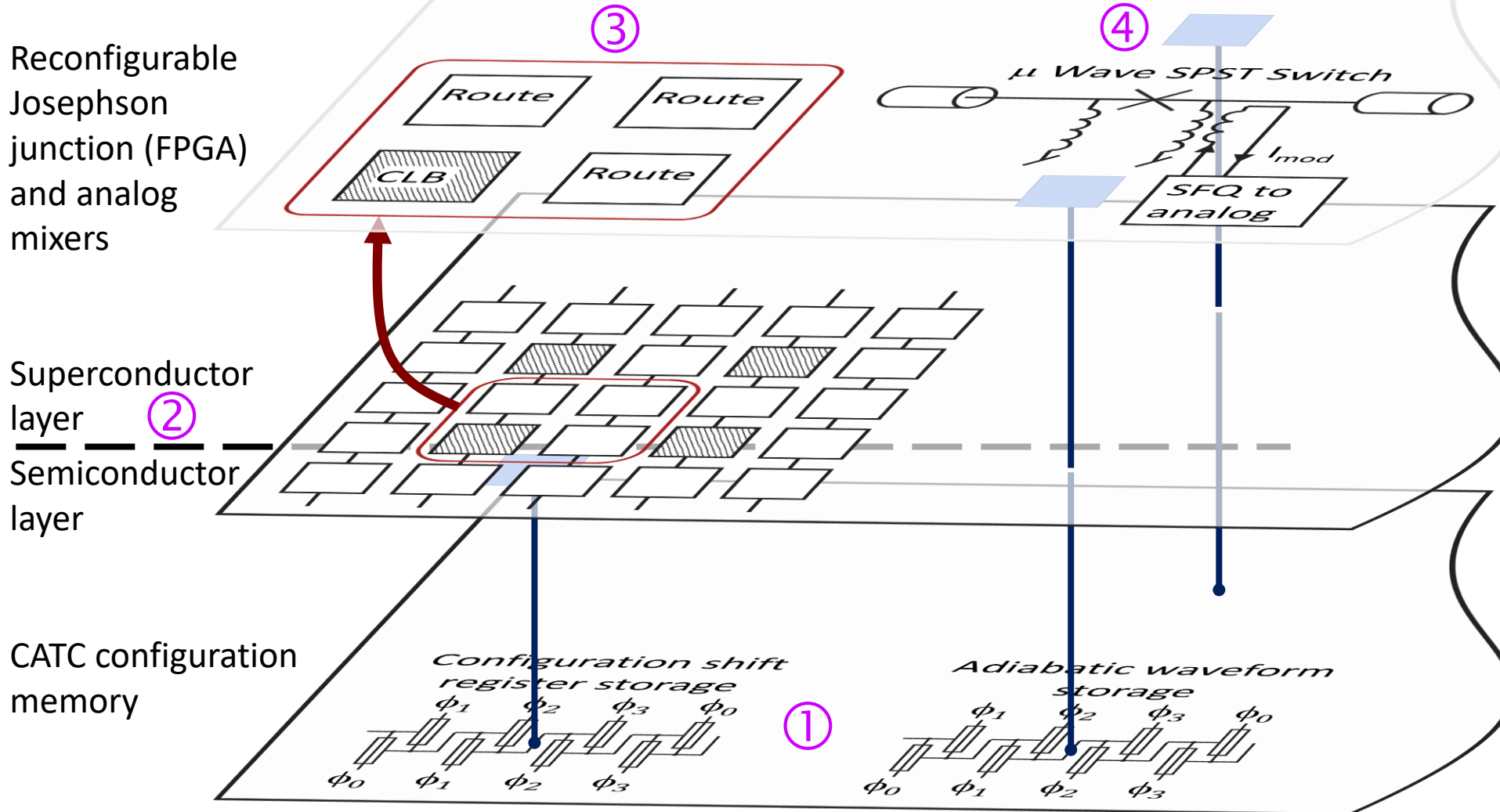Transistors/JJ Hybrid Exploits Energy-Delay-Size Tradeoffs



Conclusions

- Adiabatic circuits not new, but use case is new
 - Much of this talk could have been made 30 years ago
 - Use case, cryostat, low noise concern & Q2LAL new
- Benefits today:
 - Equivalent benefit to a 99.9% CV^2 reduction at room temperature by restructuring circuit and heat flow
 - Lower noise in terms of power, noise, and bandwidth
 - Invent (?) “perfectly adiabatic sequential logic”
- Future
 - Physical demo in quantum control use case
- For more information see <https://zettaflops.org/isrds>
 - These slides; full paper with simulation code, more