

Josephson-CMOS Hybrid Session

Erik DeBenedictis
Zettaflops LLC
April 9, 2024



Overview




- Can we use JJs and semiconductors to make a hybrid chip or module with more performance than is available in any other way?
 - Novel hybrid circuits overview and example (Erik DeBenedictis)
- Talks on applications and benefits
 - Supercomputer with JJ processor CMOS memory (Whiteley/power)
 - AI machine with JJ neurons and CMOS support (Segall/nuc. reactors)
 - Merging Semiconductor Memory with Superconducting Logic (Razmkhah/architecture for high-performance cryogenic computing systems)
- Panel and Q&A
 - 5 min Quantum computer control (SeeQC) (Mukhanov/hard problems)
 - 5 min introductions for Jamil Kawa and Nobuyuki Yoshikawa
 - Q&A with all speakers

Standing on the Shoulders of Giants



- JJs are a giant
 - JJ: ~770 GHz toggle frequency
 - Extremely energy efficient
- CMOS
 - III-V GaAs transistors: have gain at slightly over 1 THz
 - Extremely dense
- Both giants

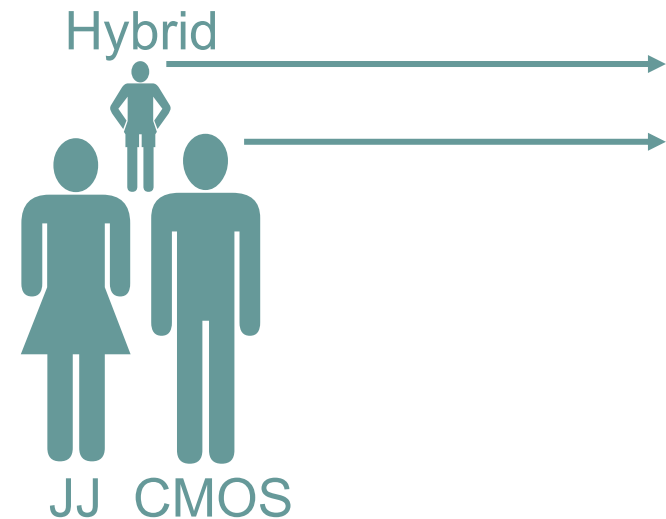- Standing on the shoulders of giants allows higher speed, throughput, # of qubits/neurons, etc.



What is a Hybrid?



- “Transparent hybrid”
 - Support circuits with both JJs and semiconductor components
 - Create schematics with components and lines/wires
- Current method
 - Support systems with both JJs and semiconductors
 - All signal paths between super- and semiconductors have a transmission line or a low-pass filter






What is a Hybrid?

- Universal hybrid
 - Support circuits with both JJs and semiconductor components
 - Create schematics with components and lines/wires



 - Current method
 - Support systems with both JJs and semiconductors
 - All signal paths between super- and semiconductors have a transmission line or a low-pass filter






What is a Hybrid?

- Universal hybrid
 - Support circuits with both JJs and semiconductor components
 - Create schematics with components and lines/wires



 
- Current method
 - Support systems with both JJs and semiconductors
 - All signal paths between super- and semiconductors have a transmission line or a low-pass filter




Standing on the Shoulders of Dwarves



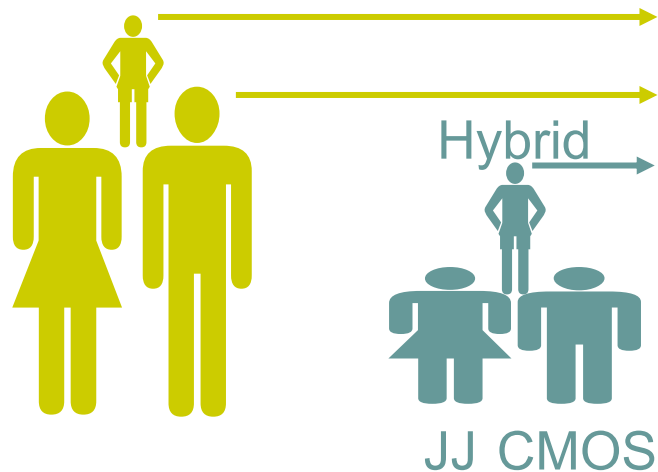- If you stand on the shoulders of dwarves, you may end up below the level of the original giants
- Need a “latency tolerant architecture”



 - Monolithic integration:
 - Superconductor Fast
 - Semiconductor Via
- Deposit semi-conductor?
- Back-end-of-line superconductor




Mine the Hybrid to Enhance CMOS or JJs



- Add variable capacitors to the JJ process
 - Variable capacitors are called varactors
 - Most CMOS processes have varactors
- Add HKI inductors to CMOS

- Example

 

Monolithic vs. Other Hybrid Fab Status



Monolithic hybrid

- Fabs: “no problem”
- Skeptics: “materials problems”
- MIT-LL made a monolithic hybrid
 - JJs and transistors worked, so no major materials problems
 - Turning on the transistors overheated the JJs and they stopped working
 - Emphatic it was a design issue
 - Verbal information only

Bumps and interposers

- MIT-LL Superconducting Multi-Chip Module (S-MCM)
- Excellent quality transmission lines

Design Principles for JJ CMOS Hybrids



Which layer for a functional block?

- If a block is too big, move it to the semiconductor base
- If a block dissipates too much heat, move it to the JJ layer
- Note: Requires a computer architect

Novel circuits spanning both layers

- Nobody has thought of them before because they could not be fabricated, so
 - Unexpected capability
 - More likely to be publishable, patentable, or a competitive differentiator



Part 2: Example of a Novel Circuit

Erik DeBenedictis

Zettaflops LLC


April 9, 2024

Reversible Semiconductor Logic, a Novel Circuit Class (I)



- CMOS circuit → reversible circuit
 - Switch logic gate circuits
 - Retain the functional block structure, busses, and long wires
- Power and clocking
 - In CMOS all energy goes in electrically and leaves as heat
 - In a reversible circuit (at 1 GHz), energy goes in during the 1st half of

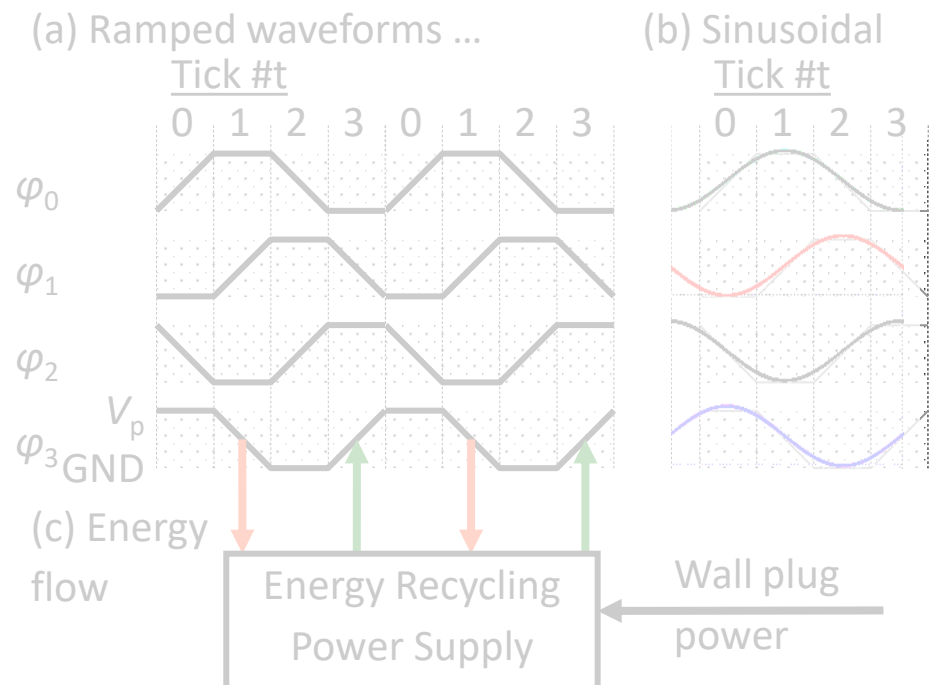- each nanosecond and 90% - 99% comes out in the 2nd
- Waveforms and energy recycling




Reversible Logic Story, with Scale up Chapter



300 K: Metal inductors


Typical diagram below; External inductor

 

(left →) Power-clock generator
(right →) external inductor

77 K: High Tc inductors

 
Geometric inductors require absence of conductors in surrounding space



(blue) array of rev. logic semiconductor chips
(gold) YBCO inductors

4 K: HKI inductors

Diagram exploded; actually monolithic
No need for empty space, so multiple layers possible

 

(yellow) HKI inductor layer
(gray) Semiconductor base


Reversible Semiconductor Logic, a Novel Circuit Class (II)



- CMOS circuit → reversible circuit
 - Switch logic gate circuits
 - Retain the functional block structure, busses, and long wires
- Power and clocking
 - In CMOS all energy goes in electrically and leaves as heat
 - In a reversible circuit (at 1 GHz), **energy goes in** during the 1st half of

each nanosecond and 90% - 99% **comes out** in the 2nd


- Waveforms and energy recycling:

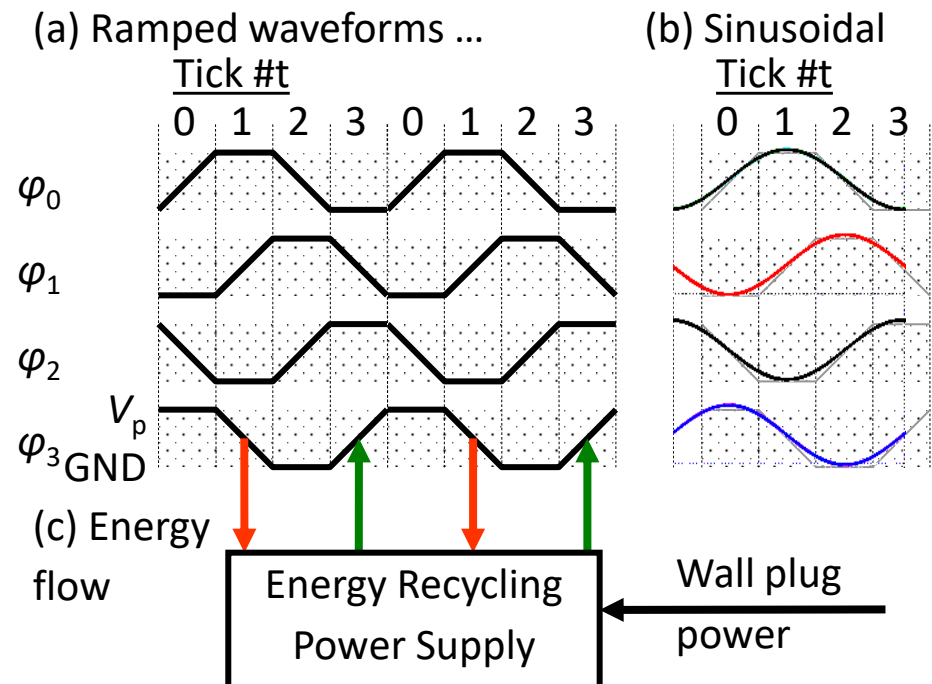

What is the Criteria for Getting Reversible Logic Unblocked?



- Diagram shows single HKI layer

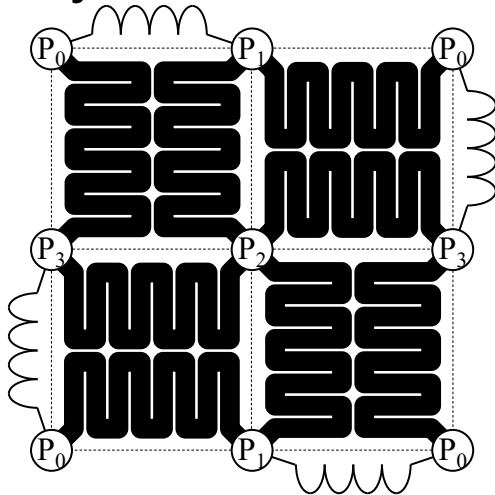

- Engineering strategy:
 - Energy/unit area must be the same for inductance at I_{\max} and capacitance at V_p .

- HKI energy content
 - SeeQC: $L_{\square} = 8.5 \text{ pH}/\square$, $I_c = 2.5 \text{ mA}/\mu\text{m} = 2500 \text{ A/m}$
 - For square dimension $s \times s$:
 - Energy in an inductor: $\frac{1}{2}LI^2 = \frac{1}{2} L_{\square} (I_c s)^2 / s^2$ (s's cancel) = $.3 \text{ nJ}/\text{chip}$ or $470 \text{ mW}/\text{chip}$ at 1.6 GHz (1 cm^2 chip)
 - Horse Ridge ($4 \times 4 \text{ mm}$): $10\text{--}140 \text{ mW} \rightarrow 62\text{--}875 \text{ mW}/\text{cm}^2$
 - So, need 2 HKI layers
 - Ref. <https://www.eetimes.com/intels-horse-ridge-ii-improves-the-control-for-quantum-computing/>


YBCO/77 K Option



A Very Raw Direction for 77 K

- Diagram includes not-to-scale YBCO inductors ref. <https://link.springer.com/content/pdf/10.1007/s00340-016-6430-z.pdf>
- YBCO inductors have plenty of power density and Q
- YBCO needs empty space around it, but could the space be on just one side?
- May be useful for DARPA LTLT
- Hats off to Robin and STAR Cryo

 77 K: High-Tc inductors Geometric inductors require absence of conductors in surrounding space – but how about on just one side?



(gold) YBCO inductors
(yellow) YBCO GND plane
(gray) semiconductor base

Conclusions on HKI for Reversible Logic



Claim: HKI “unblocks” reversible logic and it is now possible to convert practical cryo CMOS to reversible logic using JJ CMOS fab

- A hybrid chip could have regions containing reversible semiconductor logic, JJ logic, cryo CMOS logic, analog circuitry, etc.
- May increase energy efficiency over cryo CMOS by 10-100x
- Two layers of HKI possible. The method used for 3D flash may allow hundreds of layers, allowing more computational density
- I have ideas for 77 K operation, see me later
- I make no claim of an imminent room temperature solution